

The Electron's Path: Fundamental of EEE (ECE1001-Lab.)

Experiment 4 Multivibrator using IC555 Monsoon 2025

An extremely adaptable integrated circuit, the 555 timer is used in a wide range of electronic devices. Its ability to produce an oscillating waveform for many purposes allow it to be utilised as three different kinds of oscillators.

- The IC-555 operates as a precision timer with a preset duration while in its monostable mode. Applications needing exact timing, like delay circuits or pulse generators, frequently use monostable oscillators.
- When connected in bistable mode, it switches like a flip-flop. Applications requiring a steady on/off status, like toggling an output or memory storage, can benefit from this setup.
- The 555 timer IC should be set up in Astable mode to produce an oscillator circuit that is extremely steady. A highly accurate, free-running waveform is produced by this setup. Applications including tone creation, pulse-width modulation, and clock generation also frequently use it.

IC555 is an 8 pin DIP (Dual in Package) IC as shown in fig.1.

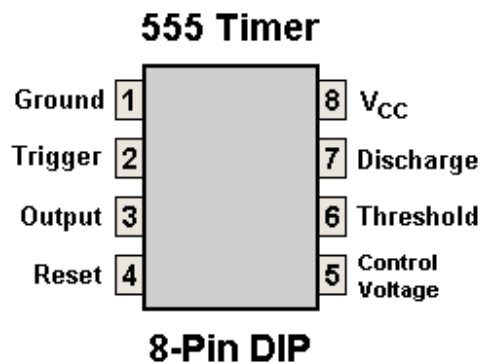


Fig. 1(a) Pin Connection of IC555 Timer

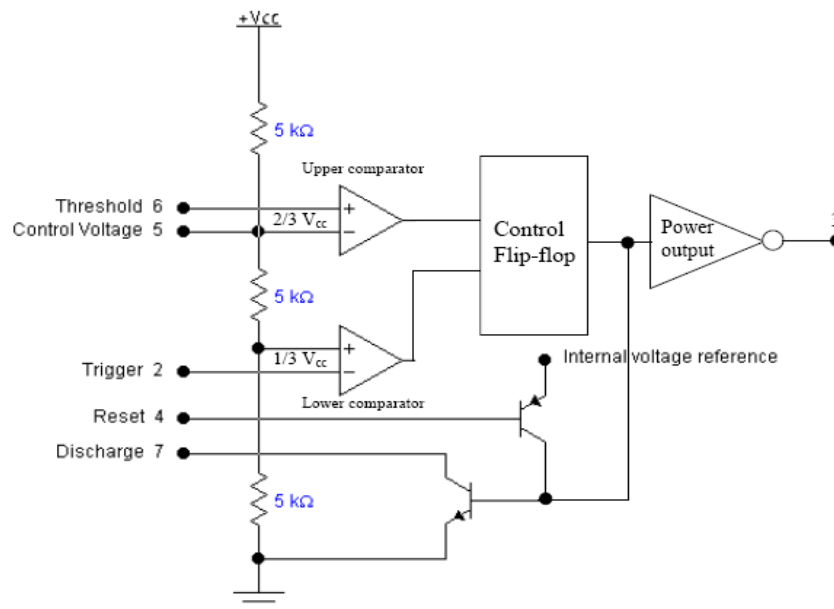


Fig. 1(b) Internal diagram of of IC555 Timer

A. Astable Multivibrator

The circuit of an Astable multivibrator is shown in **Fig. 2**. The selection of R_1 , R_2 and C is important to form the wave. The capacitor 'C' undergoes charging through series combination of R_1 & R_2 and when the voltage across the capacitor reaches $2/3$ of the supply voltage V_{cc} , pin 6 detects this condition and turns the output OFF. Hence charging time is

$$\tau_c = 0.693 (R_1 + R_2) C$$

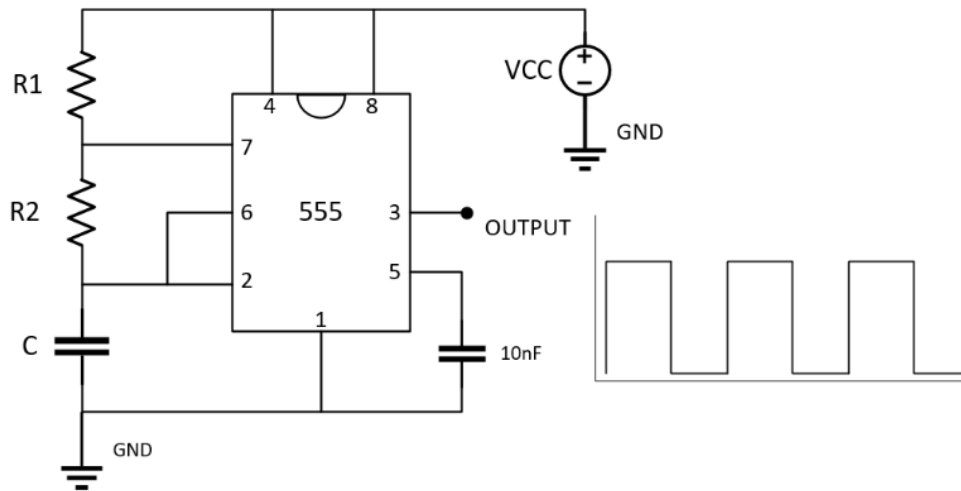


Fig. 2 Astable Multivibrator

When the output goes OFF, pin 7 switches ON and the capacitor discharges through R_2 , hence discharging time is

$$\tau_d = 0.693 (R_2) C$$

Now, as the voltage across the capacitor drops to $1/3$ of V_{cc} , pin 2 detects it and turns OFF pin 7, allowing the capacitor to start charging again. This completes the on/off cycle. This continuous charging and discharging of a capacitor give the rectangular waveform of period

$$T = \tau_c + \tau_d = T_H + T_L = 0.693 (R_1 + 2 R_2) C$$

The frequency of waveform will be $f = 1/T = 1.44 / [(R_1 + 2 R_2) C]$

Duty cycle is the ratio of time for which the output is HIGH to the total time and is given by

$$DC = T_H / T * 100 = [(R_1 + R_2) / (R_1 + 2 R_2)] * 100$$

Procedure:

1. Build the circuit of Fig. 2 on bread board. Use general purpose IC-555 Timer. Connect a ceramic capacitor of value $0.01 \mu F$ at Pin5 (control pin). Apply the DC voltage **6V** from the DC voltage source to Pin 8 (V_{cc}) & Pin4 (reset).
2. Set up the Timer 555 with $R_1 = 47.00k\Omega$, $R_2 = 47.0k\Omega$, and $C = 10\mu F$. Connect an LED with series resistor of 330Ω at output Pin 3 and ground. Connect the Ch-1 of DSO to Pin3 (output) and connect Ch-2 of DSO across the capacitor 'C' (between Pin6 & Pin1). Display the waveforms on the DSO. For the best view, set the DSO in time roll mode (*press Horiz/ select mode*). Measure the **peak-to-peak** voltage as well as the **pulse ON and OFF time** of output signal at Ch-1. Measure the **charging and discharging** time of capacitor as well as **peak to peak** voltage across capacitor 'C' at Ch-2.

3. Repeat step 2 for $C = 22\mu\text{F}$. Tabulate the peak-to-peak voltage, charging/ discharging time against the theoretically expected values. Record the waveforms and observe the LED.

Observation Table 1

$V_{CC} = \dots\dots\dots \text{V}$

C	Measured o/p Pulse Pin3				Measured across Capacitor			Theoretical o/p Pulse Pin3				Theoretical across Capacitor		
	T_H	T_L	T	V_{pp}	Dis charging time τ_d	Charging Time τ_c	$V_c = V_{\text{max}} - V_{\text{min}}$	T_H	T_L	T	V_{pp}	Dis charging time τ_d	Chargin g Time τ_c	$V_c = V_{\text{max}} - V_{\text{min}}$
10 μF														
22 μF														

B. Monostable Multivibrator

The output of the monostable multivibrator using 555 timer remains in its stable state until it gets a trigger. In monostable 555 multivibrator, when both the resistor and capacitor are shorted then this state is called as a stable state. When the voltage goes below at the second pin of the 555 IC, the o/p becomes high. This high state is called quasi stable state. When the circuit activates then the transition from a stable state to quasi stable state. Then the discharge transistor is cut off and capacitor starts charging to V_{CC} . The capacitor charging is done via the resistor R_1 with a time constant $R_1 C_1$. Hence, the voltage of the capacitor increases and finally exceeds $2/3 V_{CC}$, it will change the internal control flip flop, thereby turning off the 555 timer IC. Thus, the o/p goes back to its stable state from an unstable state.

The o/p stays in a low state until it gets a trigger i/p. This type of operation is used in push-to-operate systems. When the input is triggered, then the o/p will go to high state & comes back to its original state.

$$\tau_c = 1.1 R_1 C$$

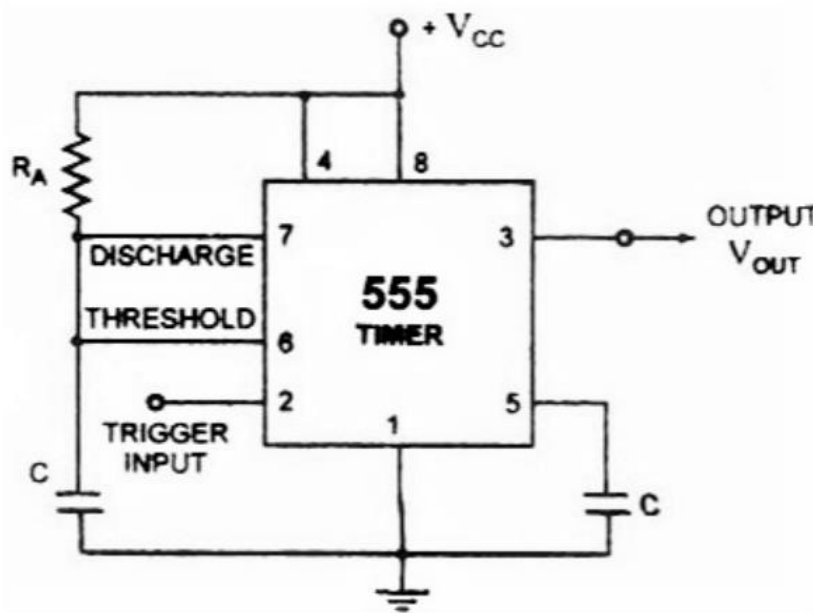


Fig. 3 Monostable Multivibrator

Procedure:

1. Build the circuit of Fig. 3 on bread board. Use general purpose IC-555 Timer. Connect a ceramic capacitor of value $0.01 \mu\text{F}$ at Pin5 (control pin). Apply the DC voltage **6V** from the DC voltage source to Pin 8 (V_{CC}) &

Pin4 (reset). Connect a wire to PIN 2(Trigger).

- Set up the Timer 555 with $R1 = 47.00k\Omega$, and $C = 100\mu F$. Connect an LED and series resistor of 330 Ohm at output Pin 3 and ground. Connect the Ch-1 of DSO to Pin3 (output) and connect Ch-2 of DSO across the capacitor 'C' (between Pin6 & Pin1). Display the waveforms on the DSO. For the best view, set the DSO in time roll mode (*press Horiz/ select mode*). Touch the trigger wire and observe LED. Measure the **peak-to-peak** voltage as well as the **pulse ON and OFF time** of output signal (Pin3) at Ch-1. Measure the **charging and discharging** time of capacitor as well as **peak to peak** voltage across capacitor 'C' at Ch-2.
- Repeat step 2 for $C = 10\mu F$. Tabulate the peak-to-peak voltage, charging/ discharging time against the theoretically expected values. Record the waveforms and observe the LED.

Observation Table 2 $V_{CC} = \dots\dots\dots V$

C	<i>Measured o/p Pulse Pin3</i>				<i>Measured across Capacitor</i>			<i>Theoretical o/p Pulse Pin3</i>				<i>Theoretical across Capacitor</i>		
	T_H	T_L	T	V_{pp}	Dis charging time τ_d	Charging Time τ_c	$V_c = V_{max} - V_{min}$	T_H	T_L	T	V_{pp}	Dis charging time τ_d	Chargin g Time τ_c	$V_c = V_{max} - V_{min}$
100 μF														
10 μF														

- Repeat step 3 with triggered input. In this step connect the **wavegen to trigger Pin2**. Apply **square waveform** of 1Hz, 1Vpp, duty cycle of 80%, offset=0V to trigger Pin2. Record the Trigger waveform (connect DSO Ch-2 at Pin 2) and o/p waveform (DSO Ch-1 at Pin 3) as well as observe the LED.

Results:

Conclusion: It must be in your words and be based on your understanding/ learning in the experiment.